

QB365 Question Bank Software

12th Physics Case study Questions Moving Charges And Magnetism For - 2024

12th Standard

Physics


SECTION A

2 x 4 = 8

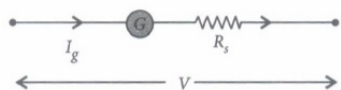1) A galvanometer can be converted into voltmeter of given range by connecting a suitable resistance R_s in series with the galvanometer, whose value is given by

$$R_s = \frac{V}{I_g} - G$$

where V is the voltage to be measured, I_g is the current for full scale deflection of galvanometer and G is the resistance of galvanometer



Series resistor (R_s) increases range of voltmeter and the effective resistance of galvanometer. It also protects the galvanometer from damage due to large current.

Voltmeter is a high resistance instrument and it is always connected in parallel with the circuit element across which potential difference is to be measured. An ideal voltmeter has infinite resistance

In order to increase the range of voltmeter n times the value of resistance to be connected in series with galvanometer is $R_s = (n - 1)G$.

(i) 10 mA current can pass through a galvanometer of resistance 25Ω . What resistance in series should be connected through it, so that it is converted into a voltmeter of 100 V?

(a) 0.975Ω (b) 99.75Ω (c) 975Ω (d) 9975Ω .

(ii) There are 3 voltmeter A, B, C having the same range but their resistance are $15,000\Omega$, $10,000\Omega$ and $5,000\Omega$ respectively. The best voltmeter amongst them is the one whose resistance is

(d) all

(a) 5000Ω (b) $10,000\Omega$ (c) $15,000\Omega$ are
equally
good

(iii) A milliammeter of range 0 to 25 mA and resistance of 10Ω is to be converted into a voltmeter with a range of 0 to 25 V. The resistance that should be connected in series will be

(a) 930Ω (b) 960Ω (c) 990Ω (d) 1010Ω

(iv) To convert a moving coil galvanometer (MCG) into a voltmeter

(a) a high resistance R is connected in parallel with MCG

(b) a low resistance R is connected in parallel with MCG

(c) a low resistance R is connected in series with MCG

(d) a high resistance R is connected in series with MCG

(v) The resistance of an ideal voltmeter is

(a) zero (b) low (c) high (d) infinity

Answer : (i) (d): A galvanometer can be converted into a voltmeter of given range by connecting a suitable high resistance R in series of galvanometer, which is given by

$$R = \frac{V}{I_g} - G = \frac{100}{10 \times 10^{-3}} - 25 = 10000 - 25 = 9975 \Omega$$

(ii) (c): An ideal voltmeter should have a very high resistance.


(iii) (c): Resistance of voltmeter = $\frac{25}{25 \times 10^{-3}} = 1000 \Omega$

$\therefore X = 1000 - 10 = 990 \Omega$


(iv) (d): To convert a moving coil galvanometer into a voltmeter, it is connected with a high resistance in series. The voltmeter is connected in parallel to measure the potential difference. As the resistance is high, the voltmeter itself does not consume current.

(v) (d): The resistance of an ideal voltmeter is infinity.

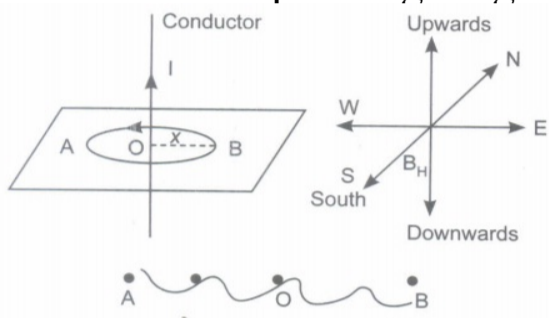2) If a straight current carrying conductor is placed as shown. Points A and B lies on west and east side of a conductor at a distance x each from the conductor. Then relate the magnetic field at A to that at B. Also draw the corresponding magnetic field lines.



Answer :

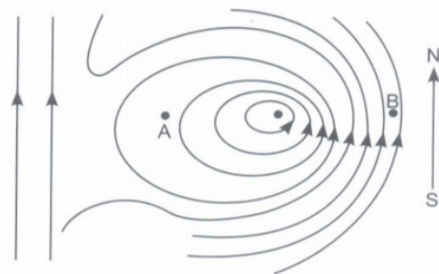

At a distance x towards east at point B, net magnetic field is due to
(i) current carrying conductor which is equal to

$$B = \frac{\mu_0 I}{2x} \text{ towards North}$$

(ii) Horizontal component of magnetic field B_H directed towards North.

$$\therefore B_B = \frac{\mu_0 I}{2x} + B_H \quad \dots\dots(i)$$

But at point A, at the same distance x ; magnetic field due to straight conductor is towards south [using Right hand thumb Rule]