


Unit 1 to 5 Five Marks Question With Answer

12th Standard

Physics

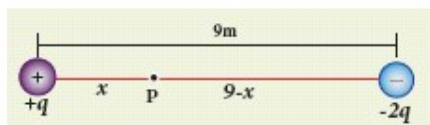- 1) Consider a point charge $+q$ placed at the origin and another point charge $-2q$ placed at a distance of 9 m from the charge $+q$. Determine the point between the two charges at which electric potential is zero.

Answer : According to the superposition principle, the total electric potential at a point is equal to the sum of the potentials due to each charge at that point. Consider the point at which the total potential zero is located at a distance x from the charge $+q$ as shown in the figure.



The total electric potential at P is zero.

$$V_{\text{tot}} = \frac{1}{4\pi\epsilon_0} \left(\frac{q}{x} - \frac{2q}{(9-x)} \right) = 0$$

Which gives $\frac{q}{x} - \frac{2q}{(9-x)}$

or $\frac{1}{x} = \frac{2}{(9-x)}$

Hence, $x=3\text{m}$

- 2) A parallel plate capacitor has square plates of side 5 cm and separated by a distance of 1 mm.
- (a) Calculate the capacitance of this capacitor.
- (b) If a 10 V battery is connected to the capacitor, what is the charge stored in any one of the plates? (The value of $\epsilon_0 = 8.85 \times 10^{-12} \text{ Nm}^2 \text{ C}^{-2}$)

Answer : (a) The capacitance of the capacitor is

$$C = \frac{\epsilon_0 A}{d} = \frac{8.85 \times 10^{-12} \times 25 \times 10^{-4}}{1 \times 10^{-3}}$$

$$= 221.2 \times 10^{-13} \text{ F}$$


$$C = 22.12 \times 10^{-12} \text{ F} = 22.12 \text{ pF}$$

(b) The charge stored in any one of the plates is $Q = CV$, Then


$$Q = 22.12 \times 10^{-12} \times 10 = 221.2 \times 10^{-12} \text{ C} = 221.2 \text{ pC}$$

- 3) For the given capacitor configuration
- (a) Find the charges on each capacitor
- (b) potential difference across them

(c) energy stored in each capacitor

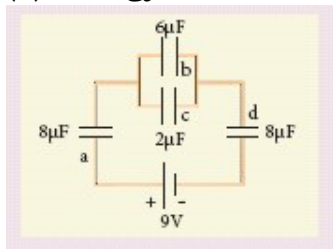

Answer :

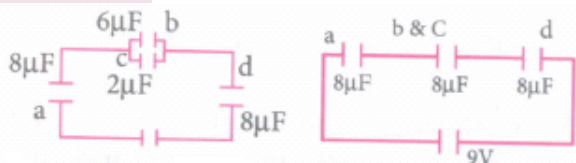

B & C are parallel so $C = (6 + 2) \mu\text{F} = 8\mu\text{F}$ Now all a, b & c, d are in series.

Effective capacitance $\frac{1}{C_s} = \frac{1}{8} + \frac{1}{8} + \frac{1}{8} = \frac{3}{8} \quad \therefore C_s = \frac{8}{3}$

a. Charges on each capacitor:

Total charges on capacitor = $q = C \cdot V$.

$$V = \frac{1}{8} \times 9 \times 10^{-6} = 24 \mu\text{C} = C$$

Charge on capacitor a = $q_a = C \cdot V$.

$$q_a = 24 \mu\text{C}$$

In case of capacitor in series the charge flowing through capacitor is same.

$$q_a = q_d = 24 \mu\text{C}$$

But across b & c, the charge is not same total are in parallel.

$$\text{Charge on b} = q_b = \frac{6}{3} \times 9 \times 10^{-6}$$

$$= 18 \mu\text{C}$$

$$\text{Charge on c} = q_c = \frac{2}{3} \times 9 \times 10^{-6}$$

$$= 6 \mu\text{C}$$

b. Potential difference across capacitor a

$$V_a = \frac{q_a}{C_a} = \frac{24 \times 10^{-6}}{8 \times 10^{-6}} = 3V$$

Potential difference across capacitor b

$$V_b = \frac{q_b}{C_b} = \frac{18 \times 10^{-6}}{6 \times 10^{-6}} = 3V$$

Potential difference across capacitor c

$$V_c = \frac{q_c}{C_c} = \frac{6 \times 10^{-6}}{2 \times 10^{-6}} = 3V$$

Potential difference across capacitor d

$$V_d = \frac{q_d}{C_d} = \frac{24 \times 10^{-6}}{8 \times 10^{-6}} = 3V$$

c. Energy stored in a $U_a = \frac{1}{2} C V^2$

$$U_a = \frac{1}{2} \times 8 \times 10^{-6} \times 3 \times 3 = 36 \mu\text{J}$$

Energy stored in b

$$U_b = \frac{1}{2} \times 6 \times 3 \times 3 \times 10^{-6} = 27 \mu\text{J}$$


$$[C_b = 6 \mu\text{F}]$$

Energy stored in c

$$U_c = \frac{1}{2} \times 2 \times 3 \times 3 \times 10^{-6} = 9 \mu\text{J}$$

$$[C_c = 2 \mu\text{F}]$$

4) From the given circuit

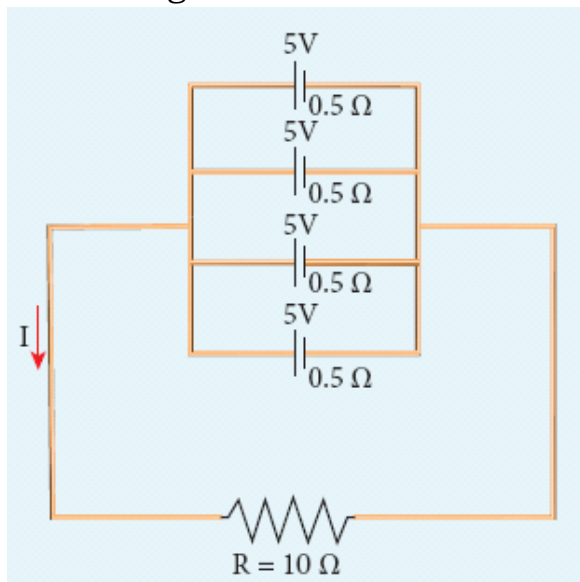

Find

- i) Equivalent emf
- ii) Equivalent internal resistance
- iii) Total current (I)
- iv) Potential difference across each cell
- v) Current from each cell

Answer : i) Equivalent emf $\xi_{eq} = 5 \text{ V}$

ii) Equivalent internal resistance,

$$R_{eq} = \frac{r}{n} = \frac{0.5}{4} = 0.125 \Omega$$

iii) total current, $I = \frac{\xi}{R_5 + \frac{r}{n}}$

$$I = \frac{5}{10 + 0.125} = \frac{5}{10.125}$$

$$I \approx 0.5 \text{ A}$$

iv) Potential difference across each cell

$$V = IR = 0.5 \times 10 = 5 \text{ V}$$

v) Current from each cell, $I' = \frac{I}{n}$

$$I' = \frac{0.5}{4} = 0.125 \text{ A}$$

5) Find the heat energy produced in a resistance of 10 Ω when 5 A current flows through it for 5 minutes.

Answer : R = 10 Ω, I = 5 A, t = 5 minutes = 5 × 60 s

$$H = I^2 R t$$

$$= 5^2 \times 10 \times 5 \times 60$$

$$= 25 \times 10 \times 300$$

$$= 25 \times 3000$$

$$= 75000 \text{ J (or) } 75 \text{ kJ}$$

6) A potentiometer wire has a length of 4 m and resistance of 20 Ω. It is connected in series with resistance of 2980 Ω and a cell of emf 4 V. Calculate the potential along the wire.

Answer : :The length of the potential wire l = 4 m

Resistors of the potential $r = 20\Omega$

Resistor connected $R = 2980\Omega$

emf of the cell $E = 4V$

To find:

potential along wire $V = ?$

Effective resistor = r & R are connected in series

$$= 2980 + 20 = (r + R)$$

$$= 3000\Omega$$

Current flowing through the wire $I = \frac{\xi}{R}$

$$I = \frac{4}{3000}$$

Potential drop across the wire $V = I \times r$

$$V = \frac{4}{3000} \times 20 = \frac{8}{300} \text{ volt}$$


$$\text{Potential gradient} = \frac{\text{Potential drop } V}{\text{length } l}$$

$$= \frac{8}{300} \times \frac{1}{4} = \frac{2}{300} = 0.66 \times 10^{-2} \text{ V m}^{-1}$$

$$\text{Potential gradient} = 0.66 \times 10^{-2} \text{ V m}^{-1}$$

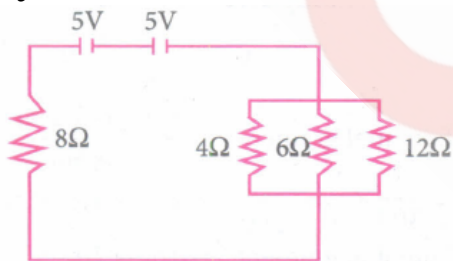- 7) Two cells each of 5V are connected in series across a 8Ω resistor and three parallel resistors of 4Ω , 6Ω and 12Ω . Draw a circuit diagram for the above arrangement. Calculate i) the current drawn from the cell (ii) current through each resistor

Answer : Equivalent resistors of R' of 4 , 6 , 12 resistors connected in parallel is given by



$$\frac{1}{R'} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12}$$

Resistor of parallel combination $R' = 2\Omega$

Total resistor i.e. 8Ω is connected in series with R'

$$R_s = 8 + R'$$

$$R_2 = 8 + 2 = 10\Omega$$

$$\therefore R_s = 10\Omega$$

Net voltage (emf) $V = 10$ [\because cells are connected in series total emf $\varepsilon + \varepsilon = 2\varepsilon$]

Circuit in through circuit $I = \frac{V}{R}$ (from ohm's law)

$$I = \frac{10}{10}; I = 1A$$

So the circuit through each cell and 80 resistor is 1A.

Potential drop across the parallel combination of three resistors is $V' = I R' = 1 \times 2 = 2 V$

$$\therefore \text{Current in } 4 \Omega \text{ resistor } I = \frac{2}{4} = 0.5A \left[I = \frac{V}{R} \right]$$

$$\text{Current in } 6 \Omega \text{ resistor, } I = \frac{2}{6} = 0.33A$$

$$\text{Current in } 12 \text{ resistor, } I = \frac{2}{12} = \frac{1}{6} = 0.17A$$

- 8) An electron moving perpendicular to a uniform magnetic field 0.500 T undergoes circular motion of radius 2.80 mm. What is the speed of electron?

Answer : Charge of an electron $q = -1.60 \times 10^{-19} C \Rightarrow |q| = 1.60 \times 10^{-19} c$

Magnitude of magnetic field $B = 0.500 T$

Mass of the electron, $m = 9.11 \times 10^{-31} kg$


Radius of the orbit, $r = 2.50 mm = 2.50 \times 10^{-3} m$

Velocity of the electron, $v = |q| \frac{rB}{m}$

$$v = 1.60 \times 10^{-19} = \frac{2.50 \times 10^{-3} \times 0.500}{9.11 \times 10^{-31}}$$

$$v = 2.195 \times 10^8 ms^{-1}$$

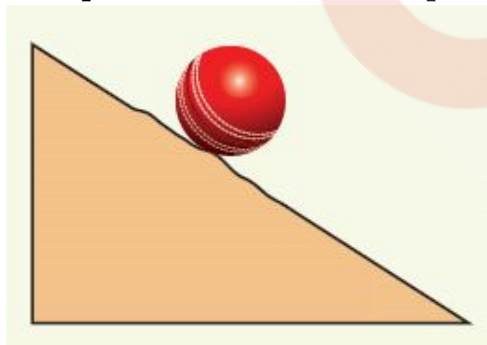- 9) mass of 100 g and radius 20 cm. A flat compact coil of wire with turns 5 is wrapped tightly around it with each turns concentric with the sphere. This sphere is placed on an inclined plane such that plane of coil is parallel to the inclined plane. A uniform magnetic field of 0.5 T exists in the region in vertically upward direction. Compute the current I required to rest the sphere in equilibrium.



Answer : The sphere is in translational equilibrium, thus

$$f_s - mg \sin\theta = 0 \quad \dots(1)$$

The sphere is in rotational equilibrium. If torques are taken about the centre of the sphere, the magnetic field produces a clockwise torque of magnitude

$$\text{i.e } \tau = mB \sin\theta \quad [\mu = NIA]$$

The frictional force (f_s) produces a anticlockwise torque of magnitude $\tau = f_s R$, where R is the radius of the sphere. Thus

$$f_s R - mB \sin\theta = 0 \quad \dots\dots(2)$$

From (1) and (2) [i.e $f_s = mg \sin\theta$ substituting in (2)]

$$mg \sin\theta R - \mu B \sin\theta mg R = \mu B$$

Substituting μ

$$mgR = NIAB$$

$$I = \frac{mgR}{NBA} \quad [\text{where } A \text{ is the area of the sphere } A = \pi R^2]$$

$$\therefore I = \frac{mg}{\pi RBN}$$

Given:

$$\text{mass of the sphere } \mu = 100\text{g} = 100 \times 10^{-3} \text{ kg}$$

$$\text{Radius of the sphere } R = 20 \text{ cm} = 20 \times 10^{-2} \text{ m}$$

$$\text{No. of turns of wire wrapped } N = 5$$

$$\text{Magnetic field } B = 0.5 \text{ T}$$

Current required to rest the sphere in equilibrium

$$I = \frac{100 \times 10^{-3} \times 10^{-2}}{\pi \times 5 \times 20 \times 10^{-2} \times 0.5}$$

$$I = \frac{2}{\pi}$$

- 10) A coil of 200 turns carries a current of 4 A. If the magnetic flux through the coil is 6×10^{-5} Wb, find the magnetic energy stored in the medium surrounding the coil.

Answer : Given: No. of turns of coil $N = 200$

Current passing through coil $I = 4\text{A}$

Magnetic flux through coil $\Phi = 6 \times 10^{-5}$ Wb

To find:

Magnetic energy stored in the medium surrounding the coil = $\frac{1}{2}LI^2$

$$\text{Self inductance } L = \frac{N\Phi}{I}$$

Solution:

$$\therefore \text{energy } UB = \frac{1}{2} \cdot N\Phi \cdot I$$

$$= \frac{1}{2} \times 200 \times 6 \times 10^{-5} \times 4$$

$$= 24 \times 10^{-3}$$