

# QB365 Question Bank Software Study Materials

## Current Electricity 50 Important 1 Marks Questions With Answers (Book Back and Creative)

12th Standard


Physics

Total Marks : 50


### Multiple Choice Question

50 x 1 = 50

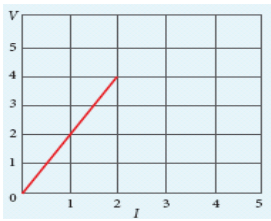- 1) The following graph shows current versus voltage values of some unknown conductor. What is the resistance of this conductor?



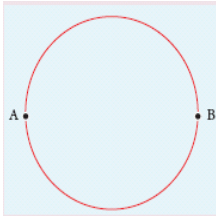- (a) **2 ohm** (b) 4 ohm (c) 8 ohm (d) 1 ohm
- 2) A wire of resistance 2 ohms per meter is bent to form a circle of radius 1m. The equivalent resistance between its two diametrically opposite points, A and B as shown in the figure is




- (a)  **$\pi\Omega$**  (b)  $\frac{\pi}{2}\Omega$  (c)  $2\pi\Omega$  (d)  $\frac{\pi}{4}\Omega$
- 3) A toaster operating at 240 V has a resistance of 120  $\Omega$ . The power is \_\_\_\_\_.  
(a) 400 W (b) 2 W (c) **480 W** (d) 240 W
- 4) A carbon resistor of  $(47 \pm 4.7)$  k  $\Omega$  to be marked with rings of different colours for its identification. The colour code sequence will be \_\_\_\_\_.  
(a) Yellow – Green – Violet – Gold (b) **Yellow – Violet – Orange – Silver** (c) Violet – Yellow – Orange – Silver  
(d) Green – Orange – Violet – Gold

- 5) What is the value of resistance of the following resistor?







- (a) **100 k  $\Omega$**  (b) 10 k  $\Omega$  (c) 1 k  $\Omega$  (d) 1000 k  $\Omega$
- 6) Two wires of A and B with circular cross section made up of the same material with equal lengths. Suppose  $R_A = 3 R_B$ , then what is the ratio of radius of wire A to that of B?  
(a) 3 (b)  $\sqrt{3}$  (c)  **$\frac{1}{\sqrt{3}}$**  (d)  $\frac{1}{3}$
- 7) A wire connected to a power supply of 230 V has power dissipation  $P_1$ . Suppose the wire is cut into two equal pieces and connected parallel to the same power supply. In this case power dissipation is  $P_2$ . The ratio  $\frac{P_2}{P_1}$  is \_\_\_\_\_.  
(a) 1 (b) 2 (c) 3 (d) **4**
- 8) In India electricity is supplied for domestic use at 220 V. It is supplied at 110 V in USA. If the resistance of a 60 W bulb for use in India is R, the resistance of a 60 W bulb for use in USA will be \_\_\_\_\_.  
(a) R (b) 2R (c)  **$\frac{R}{4}$**  (d)  $\frac{R}{2}$
- 9) In a large building, there are 15 bulbs of 40 W, 5 bulbs of 100 W, 5 fans of 80 W and 1 heater of 1 kW are connected. The voltage of electric mains is 220 V. The maximum capacity of the main fuse of the building will be \_\_\_\_\_.  
(a) 14 A (b) 8 A (c) 10 A (d) **12 A**

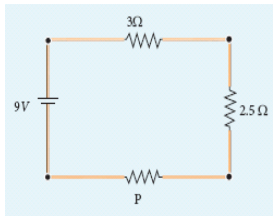- 10) There is a current of 1.0 A in the circuit shown below. What is the resistance of P ?



- (a) 1.5 Ω (b) 2.5 Ω **(c) 3.5 Ω** (d) 4.5 Ω
- 11) What is the current drawn out from the battery?
- 
- (a) 1 A** (b) 2 A (c) 3 A (d) 4 A
- 12) The temperature coefficient of resistance of a wire is 0.00125 per °C. At 20°C, its resistance is 1 Ω. The resistance of the wire will be 2 Ω at \_\_\_\_\_.
- (a) 800 °C (b) 700 °C (c) 850 °C **(d) 820 °C**
- 13) The internal resistance of a 2.1 V cell which gives a current of 0.2 A through a resistance of 10 Ω is \_\_\_\_\_.
- (a) 0.2 Ω **(b) 0.5 Ω** (c) 0.8 Ω (d) 1.0 Ω
- 14) A piece of copper and another of germanium are cooled from room temperature to 80 K. The resistance of \_\_\_\_\_.
- (a) each of them increases (b) each of them decreases (c) copper increases and germanium decreases  
**(d) copper decreases and germanium increases**
- 15) In Joule's heating law, when R and t are constant, if the H is taken along the y axis and  $I^2$  along the x axis, the graph is \_\_\_\_\_.
- (a) straight line** (b) parabola (c) circle (d) ellipse
- 16) An electron gun in a TV shoots out a beam of electrons. The beam current is  $10\mu\text{A}$ . The charge that strikes the screen in 1 minute is \_\_\_\_\_.
- (a)  $+600\mu\text{C}$  **(b)  $-600\mu\text{C}$**  (c)  $+10\mu\text{C}$  (d)  $-10\mu\text{C}$
- 17) A metallic block has no potential difference applied across it, then the mean velocity of free electrons is \_\_\_\_\_.
- (a) proportional to T (b) proportional for  $\sqrt{T}$  (c) finite but independent of temperature **(d) zero**
- 18) In an electrical arrangement as shown the equivalent resistance between X and Y will be
- 
- (a) 158.75Ω **(b) 118.75Ω** (c) 218.75Ω (d) 318.75Ω
- 19) A square aluminum rod is 1 m long and 5 mm on edge. What must be the radius of another aluminum rod whose length is 1 m and which has the same resistance as that of square Aluminum rod?
- (a) 1.4 mm **(b) 2.8 mm** (c) 4.2 mm (d) 5.6 mm
- 20) Kirchoff's I law i.e,  $\sum i = 0$  at a junction, deals with the conservation of \_\_\_\_\_.
- (a) charge** (b) energy (c) momentum (d) angular momentum
- 21) The potential gradient of the potentiometer wire depends on \_\_\_\_\_.
- (a) only on the current that flows (b) only on the resistance per unit length of the wire **(c) both the above mentioned**  
(d) none of the above

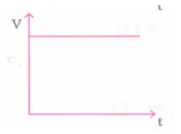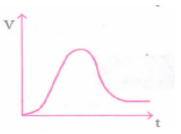- 22) The conductivity is the reciprocal of \_\_\_\_\_.
- (a) resistance    **(b) specific resistance**    (c) conductance    (d) potential difference
- 23) Nichrome wire is used as the heating element because it has \_\_\_\_\_.
- (a) low specific resistance    (b) low melting point    **(c) high specific resistance**    (d) high specific resistance
- 24) An ideal cell is connected to a capacitor through a voltmeter. The reading  $V$  of the voltmeter is plotted against time. Which of the following best represents the resulting curve?
- (a)     **(b)**     (c)     (d) 
- 25) By increasing the temperature, the specific resistance of a conductor and a semiconductor \_\_\_\_\_.
- (a) increases for both    **(b) increases, decreases respectively**    (c) decreases for both  
(d) decreases, increases respectively
- 26) The unit of electromotive force is \_\_\_\_\_
- (a) joule    (b) newton    (c) coulomb    **(d) volt**
- 27) A resistance of a metal wire of length  $AB$  is  $2\Omega$ . Another wire of length  $PQ$  of the same metal with twice the diameter of the wire  $AB$  is found to have the same resistance of  $2\Omega$ . What is the length of  $PQ$ ?
- (a) 4 AB**    (b) 2 AB    (c) 1 AB    (d) 6 AB
- 28) These are behaving like thermistor \_\_\_\_\_.
- (a) Insulators and conductors    (b) Semiconductors and conductors    (c) Conductors and alloys  
**(d) Insulators and semiconductors**
- 29) The heat developed in half a minute resistor of resistance  $5\Omega$  is 15,000 joule. The current through the resistor is \_\_\_\_\_
- (a) 5 A    (b) 100 A    (c) 40A    **(d) 10A**
- 30) The potentiometer wire is made of \_\_\_\_\_
- (a) Manganin**    (b) Copper    (c) Aluminium    (d) Nichrome
- 31) The tolerance of silver ring in resistors is \_\_\_\_\_
- (a) 5%    **(b) 10%**    (c) 20 %    (d) 2 %
- 32) Resistance of a metal wire of length 10 cm is 2. If the wire is stretched uniformly to 50 cm the resistance is \_\_\_\_\_
- (a)  $25\Omega$     (b)  $10\Omega$     (c)  $5\Omega$     **(d)  $50\Omega$**
- 33) The specific resistance for the insulators is in the range of \_\_\_\_\_
- (a)  $10^{-6}$ - $10^{-8}\Omega m$     **(b)  $10^8$ - $10^{14}\Omega m$**     (c)  $10^{-8}$ - $10^{-14}\Omega m$     (d)  $10^{-8}$ - $10^{14}\Omega m$
- 34) The specific resistance of silver is \_\_\_\_\_
- (a)  $1.7 \times 10^{-8}\Omega m$     (b)  $1.8 \times 10^{-7}\Omega m$     (c)  $1.6 \times 10^8\Omega m$     **(d)  $16 \times 10^{-9}\Omega m$**
- 35) The temperature at which normal conductor is converted into super conductor is \_\_\_\_\_
- (a) neutral temperature    (b) transition temperature    (c) critical temperature    **(d) both (b) and (c)**
- 36) The first theoretical explanation superconductivity was given by \_\_\_\_\_
- (a) BSC theory    **(b) BCS theory**    (c) SBC theory    (d) None
- 37) The temperature coefficient of resistance is positive \_\_\_\_\_.
- (a) for metals    (b) for insulators    **(c) (a) and (b)**    (d) all the above

- 38) In Kirchoff's II law the current in clockwise direction is taken as\_\_\_\_\_
- (a) positive** (b) negative (c) neutral (d) no direction
- 39) The small error in Meter Bridge experiment due to end resistance will be eliminated by\_\_\_\_\_
- (a) by interchanging the resistances** (b) by interchanging the galvanometer and jockey  
(c) by interchanging the battery and the jockey (d) without changing the resistances
- 40) Potentiometer is an instrument used for the measurement of\_\_\_\_\_
- (a) current** (b) resistance (c) capacitance (d) potential difference
- 41) The equivalent resistance in series combination is \_\_\_\_\_.
- (a) Larger than the smallest resistance **(b) Larger than the largest resistance** (c) Smaller than the largest resistance  
(d) Smaller than the smallest resistance
- 42) If the length of conductor is halved, then its conductivity would be \_\_\_\_\_.
- (a) quadrupled (b) halved (c) double **(d) unchanged**
- 43) If the resistance of a coil is 3 ohm at 20 °C and  $\alpha = 0.004/^\circ\text{C}$  then its resistance at 100 °C is \_\_\_\_.
- (a)  $1.98\Omega$  **(b)  $3.96\Omega$**  (c)  $7.92\Omega$  (d)  $39.6\Omega$
- 44) The unit of mobility of free electron is \_\_\_\_\_.
- (a)  $\text{Vm}^{-1}\text{s}^{-2}$  (b)  $\text{m}^2\text{Vs}^{-1}$  **(c)  $\text{m}^2\text{V}^{-1}\text{s}^{-1}$**  (d)  $\text{m}^2\text{V}^{-1}\text{s}$
- 45) If the length of the conductor is doubled and its area, is reduced to half of its value, then its resistance would be \_\_\_\_\_.
- (a) increased by two times (b) increased by four times **(c) decreased by four times** (d) decreased by two times
- 46) RMS voltage and frequency of  $v = 230 \sin(314 t)$  A.C. source.
- (a) 162.6V, 50Hz** (b) 230V, 50Hz (c) 230V, 60Hz (d) 162.6V, 25Hz
- 47) Dimension of Resistance is \_\_\_\_\_.
- (a)  $\text{ML}^2\text{T}^{-3}\text{A}^{-2}$**  (b)  $\text{ML}^2\text{T}^{-1}\text{A}^{-1}$  (c)  $\text{ML}^2\text{T}^{-2}\text{A}^{-3}$  (d)  $\text{ML}^2\text{T}^{-1}\text{A}^{-2}$
- 48) Kirchoff's I and II laws are based on conservation of \_\_\_\_\_.
- (a) charge and energy** (b) energy and charge (c) energy and voltage (d) energy and current
- 49) If a current of 7.5 A is maintained in a wire for 45 s then the charge flowing through the wire is :
- (a) 6 C** (b) 365.5 C (c) 3 C (d) 337.5 C
- 50) For the fuse wire, which of the following characteristic is immaterial?
- (a) Radius (b) Resistivity **(c) Length** (d) None of these